

CprE 381 – Computer Organization and Assembly-Level Programming

Lab-04 Report

Student Name Mason Walls

Section / Lab Time Section 6, Thurs 4:10 to 6:00

Submit a typeset pdf version of this on Canvas by the due date. Refer to the highlighted language in the Lab-04 instructions for the context of the following questions.

- a. [Prelab] Based on the waveforms, provide a description in your own words of how this component operates. This can be in the form of a textual description, flow chart, or state machine

- b. [Part 1 (a)] What are the MIPS instructions that require some value to be sign extended? What are the MIPS instructions that require some value to be zero extended?


Sign extended: sw, slti, sh

Zero extended: ori, andi

- c. [Part 1 (b)] what are the different 16-bit to 32-bit “extender” components that would be required by a MIPS processor implementation?

Zero extender and sign extender

- d. [Part 1 (d)] Waveform.

 



- e. [Part 2 (b)] Provide a 2-3 sentence description of each of the individual ports (both generic and regular).

Clk is the clock input which enables writing. Addr is the address that we are writing to, data is what is going to be stored, we is the write enable input. Q is the data output for reading.

- f. [Part 2 (c)] Waveform.

| | | | |
|---|------|--------------|----------|
| + | (29) | 32'hXXXXXXXX | XXXXXXXX |
| + | (28) | 32'hXXXXXXXX | XXXXXXXX |
| + | (27) | 32'hXXXXXXXX | XXXXXXXX |
| + | (26) | 32'hXXXXXXXX | XXXXXXXX |
| + | (25) | 32'hXXXXXXXX | XXXXXXXX |
| + | (24) | 32'hXXXXXXXX | XXXXXXXX |
| + | (23) | 32'hXXXXXXXX | XXXXXXXX |
| + | (22) | 32'h0000B000 | 0000B000 |
| + | (21) | 32'h0000A000 | 0000A000 |
| + | (20) | 32'hXXXXXXXX | XXXXXXXX |
| + | (19) | 32'hXXXXXXXX | XXXXXXXX |
| + | (18) | 32'hXXXXXXXX | XXXXXXXX |
| + | (17) | 32'hXXXXXXXX | XXXXXXXX |
| + | (16) | 32'hXXXXXXXX | XXXXXXXX |
| + | (15) | 32'hXXXXXXXX | XXXXXXXX |
| + | (14) | 32'hXXXXXXXX | XXXXXXXX |
| + | (13) | 32'hXXXXXXXX | XXXXXXXX |
| + | (12) | 32'hXXXXXXXX | XXXXXXXX |
| + | (11) | 32'hXXXXXXXX | XXXXXXXX |
| + | (10) | 32'hXXXXXXXX | XXXXXXXX |
| + | (9) | 32'h0000000A | 0000000A |
| + | (8) | 32'hFFFFFFF7 | FFFFFFF7 |
| + | (7) | 32'h00000008 | 00000008 |
| + | (6) | 32'hFFFFFFF9 | FFFFFFF9 |
| + | (5) | 32'h00000006 | 00000006 |
| + | (4) | 32'hFFFFFFFB | FFFFFFFB |
| + | (3) | 32'h00000004 | 00000004 |
| + | (2) | 32'hFFFFFFFD | FFFFFFFD |
| + | (1) | 32'h00000002 | 00000002 |
| + | (0) | 32'h00000001 | 00000001 |

 


 

- g. [Part 2 (d)] Briefly describe how the waveforms for this mem.vhd module differ from those that you analyzed as part of the pre-lab.
The wave form differs because we do not have a byte enable line. We also do not read and write at the same time so there is not as much overlap. Each cycle is done one after another
- h. [Part 3 (a)] what control signals will need to be added to the simple processor from Lab #3? How do these control signals correspond to the ports on the mem.vhd component analyzed in problem 2)?

We will need to add a mux select for the alu and memory outputs being fed into register file's data port, as well as a sign/zero extend signal for the immediate value into the alu.

 - i. [Part 3 (b)] Draw a schematic of a simplified MIPS processor consisting only of the base components used in Lab #3, the extender component described in problem (1), and the data memory from problem (2).



- k. [Feedback] You must complete this section for your lab to be graded. Write down the first response you think of; I expect it to take roughly 5 minutes (do not take more than 10 minutes).

- i. How many hours did you spend on this lab?

| Task | During lab time | Outside of lab time |
|---------------------|-----------------|---------------------|
| Reading lab | .25 | 0 |
| Pencil/paper design | 1 | .25 |
| VHDL design | 2 | .25 |
| Assembly coding | 0 | 0 |
| Simulation | .5 | .25 |
| Debugging | .25 | .25 |
| Report writing | 0 | .75 |
| Other: | 0 | 0 |
| Total | 4 | 1.75 |

- ii. If you could change one thing about the lab experience, what would it be? Why?
Better explanation of how the alu, register file, and memory are supposed to mesh together. Had to ask a TA and it was still rather confusing at times
- iii. What was the most interesting part of the lab?
Being able to mesh together all of the parts of lab and be able to store it into ram